

# Discrete Logic Gates Guide

Jesse Hamner

## Abstract

This guide contains the parts lists and schematics for each of the logic gates included in the repository. All fundamental logic gates are included, as are several more complex gates. These gates are in no way designed to be efficient or cost-effective; they are intended as functional, educational-only components. Some of the boards require surface-mount components, to reduce cost and size, but none of the discrete logic gates do. That is, some of the infrastructure pieces, and “move things along more smoothly” pieces, require SMD soldering, but workarounds for these units exist, using through-hole components and a solderless breadboard (see text for more). The bills of materials (BOMs) were created with cost in mind, but very few through-hole P-type MOSFETs are available, and they cost over USD\$0.30 apiece, as of this writing. The N-type MOSFETs are much cheaper, but the costs can add up quickly if you are building XOR gates. Especially because of the cost of through-hole P-type MOSFETs, some components will be SMD-only until demand rises for through-hole solderable versions.

**Keywords:** STEM; education; electronics; elementary education; soldering.



A second grader soldering through-hole headers and components.



This work is licensed under a [Creative Commons Attribution-NonCommercial-ShareAlike 4.0 International License](https://creativecommons.org/licenses/by-nc-sa/4.0/).

# 1 OR Gate

Making an OR gate is almost trivially easy – you can even make it without transistors. The simplest OR gate is two inputs, each into a diode, and the diodes tied together as an output. It's not a very good OR gate, but it works. Transistor-transistor logic (TTL) OR gates are more recognizable, but BJT transistors need a significant amount of resistance on the gate and the output to drag the voltage low enough to count as a zero. Typically, a CMOS OR gate is a NOR gate coupled with a NOT gate, since both of these gates can be made with CMOS circuits and therefore save energy and reduce heat.

# 2 AND Gate

Two versions exist: MOSFET and TTL. Similar to the OR gate, CMOS AND gates are usually NAND and NOT gates on the output. The TTL version is only for demonstration.

# 3 NOT Gate

The NOT, NOR, and NAND gates all use [Complementary Metal Oxide Semiconductor](#) (CMOS) construction, because of the low power consumption and clarity of output voltages. The NOT gate, in particular, is very elegant in CMOS construction: when the input line is low (logic 0), the P-type transistor is open and the N-type transistor is closed, meaning all voltage is available via the P-type FET, cannot flow to ground because the N-type FET is blocked off, and so goes to the output. The reverse (the *complement*) happens when the input line is high (logic 1): the P-type gate is closed, and the N-type gate is open, preventing the flow of current from the voltage input, and exposing ground voltage (zero volts) to the output.

Part	Value	Device	Package	Description
JP1	Input/Output	pin header	1x2 header	Standard 2-pin 0.1" header
JP2	$V_{in}$ & $GND$	pin header	1x2 header	Standard 2-pin 0.1" header
Q1	ZVP3306A	transistor	TO-92-3	P-type MOSFET transistor
Q2	BS270	transistor	TO-92-3	N-type MOSFET transistor
R1	100K	small resistor	0204/5	Pull-down resistor
R2	10K (10,000 $\Omega$ )	Small resistor	0204/5	Current-limiting resistor
R3	100R (100 $\Omega$ )	$\frac{1}{4}$ -watt resistor	0207/7	Current-limiting resistor

## 4 NOR Gate

CMOS

## 5 NAND Gate

CMOS

## 6 XOR Gate

While it is possible to make an XOR gate with less than 12 transistors, this version uses 12, because it becomes possible to see the individual gates in the schematic and even the board layout. This board also uses CMOS topology, which improves its speed and output response.

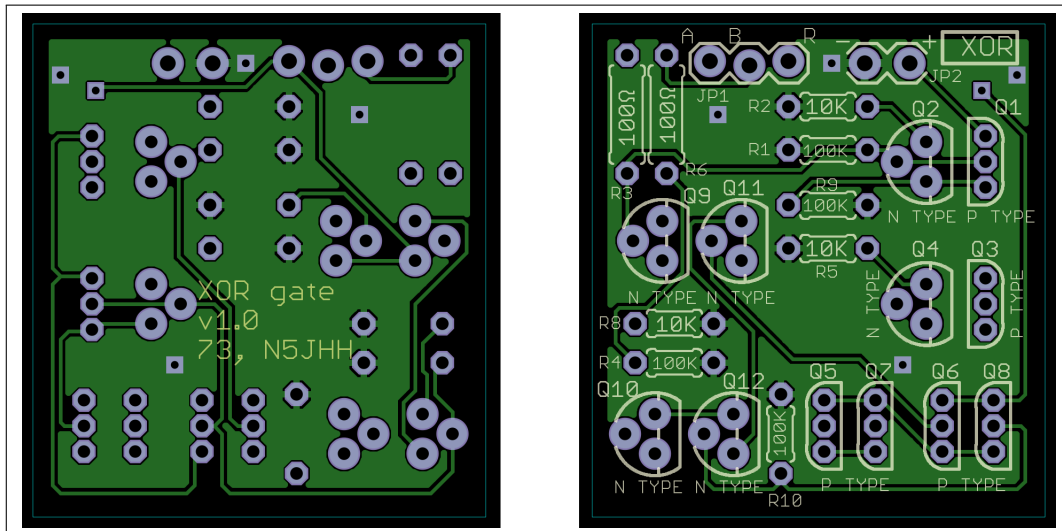


Figure 1: A 12-transistor eXclusive-OR (XOR) gate. This design uses complementary transistors (CMOS).

## 7 Full Adder

Uses SMD components, with one logic gate per IC. While it is possible to get full adders on a single chip, these boards maintain the relative ease of “following the electrons” from gate to gate, without the cost or size requirements to achieve 4 or more full adders with discrete transistors. Participants would be well-served to make at least one full adder from discrete-component gates, just to prove that it works to themselves, but perhaps use these full adder boards to make the “calculator.”

The added difficulty of SMD soldering is obvious, and including the SMD design reflects a space- and cost-conscious approach, rather than the expectation that all novices should be able to solder surface-mount components. These are not the easiest to surface mount, but the author has had success hand-soldering 0603 and even 0402-sized components without a microscope, so with practice, the larger 0805 and SOT-23 pattern components are not a challenge.

## 8 Toggle Switch Board

a bank of 4 toggle switches, with LED indicators built in. This design requires SMD soldering, but can be duplicated without much pain on a breadboard. Furthermore, the LED indication can be omitted with no loss of functionality. In other words, while it is easier to solder the SMD components first, it is at least possible to solder them after installing the switches. These designs include some “nice-to-haves” like capacitors on the data inputs and power supply. Especially in winter, stray capacitance can create some odd effects, so these extra components provide a measure of reliability and help ensure sane behavior of the circuits.

Part	Value	Package	Description
<input type="checkbox"/> C1	0.1 $\mu$ F	C0805	capacitor
<input type="checkbox"/> C2	0.1 $\mu$ F	C0805	capacitor
<input type="checkbox"/> C3	0.1 $\mu$ F	C0805	capacitor
<input type="checkbox"/> C4	0.1 $\mu$ F	C0805	capacitor
<input type="checkbox"/> JP1		1 $\times$ 2 Header	Standard 2-pin 0.1 header
<input type="checkbox"/> JP2		1 $\times$ 4 Header	Header 4
<input type="checkbox"/> LED0		0805	LED
<input type="checkbox"/> LED1		0805	LED
<input type="checkbox"/> LED2		0805	LED
<input type="checkbox"/> LED3		0805	LED
<input type="checkbox"/> Q0	2N2222	SOT23	NPN TRANSISTOR
<input type="checkbox"/> Q1	2N2222	SOT23	NPN TRANSISTOR
<input type="checkbox"/> Q2	2N2222	SOT23	NPN TRANSISTOR
<input type="checkbox"/> Q3	2N2222	SOT23	NPN TRANSISTOR
<input type="checkbox"/> R1	330 $\Omega$	M0805	resistor
<input type="checkbox"/> R2	330 $\Omega$	M0805	resistor
<input type="checkbox"/> R3	330 $\Omega$	M0805	resistor
<input type="checkbox"/> R4	330 $\Omega$	M0805	resistor
<input type="checkbox"/> R5	1K	M0805	resistor
<input type="checkbox"/> R6	1K	M0805	resistor
<input type="checkbox"/> R7	1K	M0805	resistor
<input type="checkbox"/> R8	1K	M0805	resistor
<input type="checkbox"/> S0	SPDT	SLIDESWITCHSPDT	Single pole single-throw slide switch
<input type="checkbox"/> S1	SPDT	SLIDESWITCHSPDT	Single pole single-throw slide switch
<input type="checkbox"/> S2	SPDT	SLIDESWITCHSPDT	Single pole single-throw slide switch
<input type="checkbox"/> S3	SPDT	SLIDESWITCHSPDT	Single pole single-throw slide switch

## 9 8-LED Indicator

Again, this indicator bank uses surface mount components, primarily to economize on cost of transistors and PCBs. It is very easy to rig up many LED indicators on a solderless breadboard, should SMD soldering be daunting to the end-users. However, as above, hand-soldering these components is not unreasonably hard. This board is available here because of its general usefulness, and because it appears in some document figures. Admittedly, these boards are best soldered in a reflow oven, using solder paste and a solder stencil. See Figure 2 as evidence a 9-year-old can do that with some care and patience.

Part	Value	Package	Description
<input type="checkbox"/> JP1	M10LOCK	1X10_LOCK	Header 10
<input type="checkbox"/> LED0	GRN	CHIP-LED0805	LED
<input type="checkbox"/> LED1	GRN	CHIP-LED0805	LED
<input type="checkbox"/> LED2	GRN	CHIP-LED0805	LED
<input type="checkbox"/> LED3	GRN	CHIP-LED0805	LED
<input type="checkbox"/> LED4	GRN	CHIP-LED0805	LED
<input type="checkbox"/> LED5	GRN	CHIP-LED0805	LED
<input type="checkbox"/> LED6	GRN	CHIP-LED0805	LED
<input type="checkbox"/> LED7	GRN	CHIP-LED0805	LED
<input type="checkbox"/> Q1	2N3904	SOT23	BJT NPN transistor
<input type="checkbox"/> Q2	2N3904	SOT23	BJT NPN transistor
<input type="checkbox"/> Q3	2N3904	SOT23	BJT NPN transistor
<input type="checkbox"/> Q4	2N3904	SOT23	BJT NPN transistor
<input type="checkbox"/> Q5	2N3904	SOT23	BJT NPN transistor
<input type="checkbox"/> Q6	2N3904	SOT23	BJT NPN transistor
<input type="checkbox"/> Q7	2N3904	SOT23	BJT NPN transistor
<input type="checkbox"/> Q8	2N3904	SOT23	BJT NPN transistor
<input type="checkbox"/> RA1	220 $\Omega$	CAY16-J4	Resistor Network with 4 resistors, 1206 package
<input type="checkbox"/> RA2	100K	CAY16-J4	Resistor Network with 4 resistors, 1206 package
<input type="checkbox"/> RA3	220 $\Omega$	CAY16-J4	Resistor Network with 4 resistors, 1206 package
<input type="checkbox"/> RA4	100K	CAY16-J4	Resistor Network with 4 resistors, 1206 package



Figure 2: An elementary school student placing 0805 and SOT-23 components on to a PCB with solder paste already applied through a metal stencil. The solder paste helps hold components in place until they are soldered in a reflow oven. Reflow ovens can be obtained as cheaply as USD 200.